

**DIGITAL DESIGN CS223**

**SECTION 02**


**LAB 04**

**Sümeyye ACAR**

**22103640**

**16.05.2023**
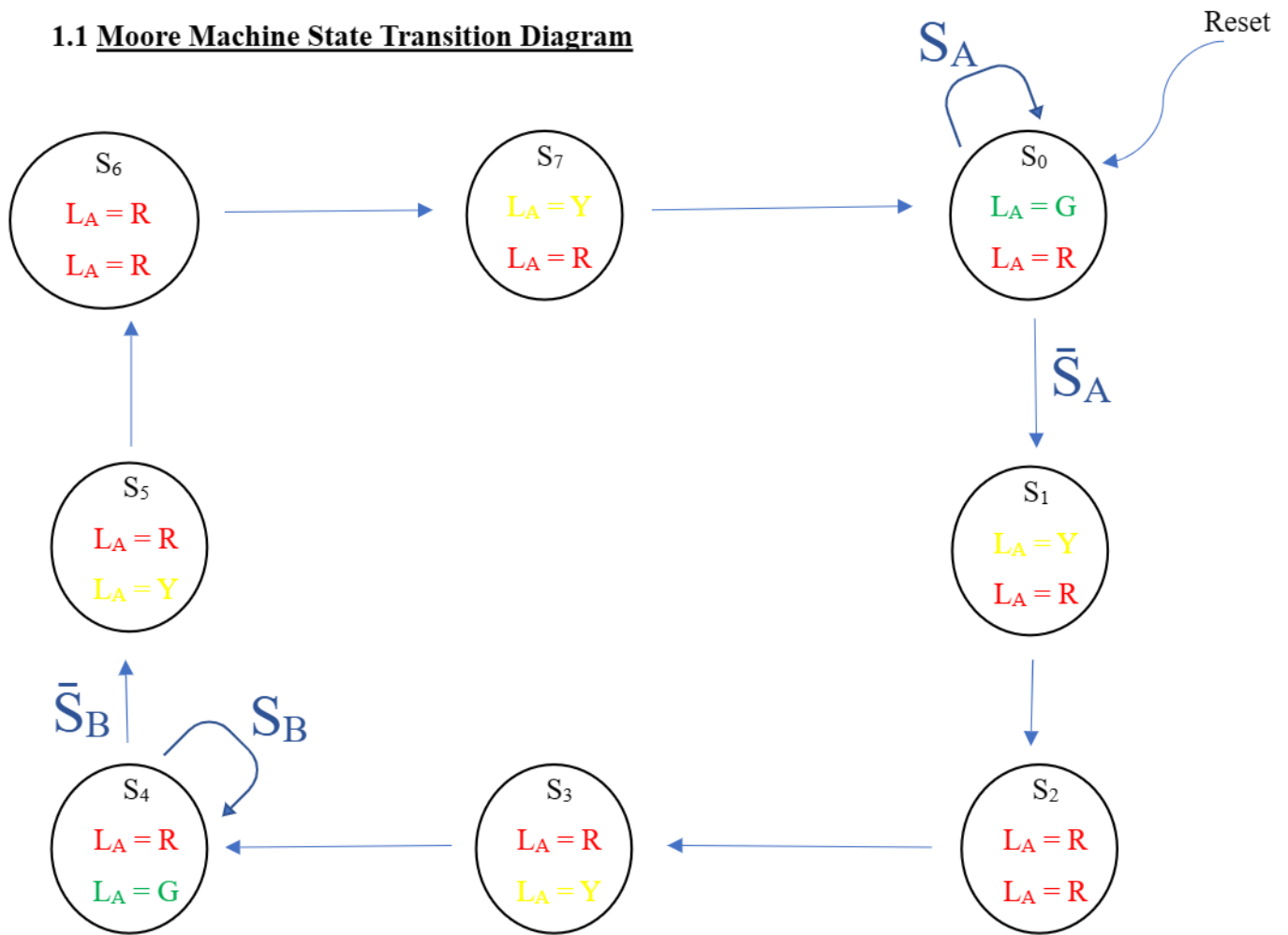
## 1.1 Moore Machine State Transition Diagram



## 1.2 State Encoding

$S_2$	$S_1$	$S_0$	State
0	0	0	$S_0$
0	0	1	$S_1$
0	1	0	$S_2$
0	1	1	$S_3$
1	0	0	$S_4$
1	0	1	$S_5$
1	1	0	$S_6$
1	1	1	$S_7$

### 1.3 State Transition Table

Current State			Input		Next State		
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	S <sub>A</sub>	S <sub>B</sub>	N <sub>2</sub>	N <sub>1</sub>	N <sub>0</sub>
0	0	0	1	X	0	0	0
0	0	0	0	X	0	0	1
0	0	1	X	X	0	1	0
0	1	0	X	X	0	1	1
0	1	1	X	X	1	0	0
1	0	0	X	1	1	0	0
1	0	0	X	0	1	0	1
1	0	1	X	X	1	1	0
1	1	0	X	X	1	1	1
1	1	1	X	X	0	0	0

### 1.4 Output Table

State			Output (L <sub>A</sub> )			Output (L <sub>B</sub> )		
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	L <sub>A2</sub>	L <sub>A1</sub>	L <sub>A0</sub>	L <sub>B2</sub>	L <sub>B1</sub>	L <sub>B0</sub>
0	0	0	0	1	1	1	1	1
0	0	1	0	0	1	1	1	1
0	1	0	1	1	1	1	1	1
0	1	1	1	1	1	0	0	1
1	0	0	1	1	1	0	1	1
1	0	1	1	1	1	0	0	1
1	1	0	1	1	1	1	1	1
1	1	1	0	0	1	1	1	1

111 = RED  
011 = GREEN  
001 = YELLOW

## 1.5 Equations

Next State:

$$N_2 = \bar{S}_2 S_1 S_0 + S_2 \bar{S}_1 + S_2 S_1 \bar{S}_0$$

$$N_1 = S_1 \oplus S_0$$

$$N_0 = \bar{S}_2 \bar{S}_1 \bar{S}_0 \bar{S}_A + S_2 \bar{S}_1 \bar{S}_0 \bar{S}_B + S_1 \bar{S}_0$$

Output:

$$L_{A2} = S_2 S_1 \bar{S}_0 + (S_2 \oplus S_1)$$

$$L_{A1} = \bar{S}_0 + (S_2 \oplus S_1)$$


$$L_{A0} = 1$$

$$L_{B2} = (S_2 \oplus \bar{S}_1) + \bar{S}_2 S_1 \bar{S}_0$$

$$L_{B1} = \bar{S}_0 + (\bar{S}_2 \oplus S_1)$$

$$L_{B0} = 1$$
 
## **2.0 Finite State Machine Schematic**



### **3.0 Number of Flip-Flops**

The number of needed flip-flops is **3** because the number of states which is 8. 8 states can be represented with 3-bit binary numbers; so, 3 flip-flops will be needed.

---

## **4.0 SystemVerilog Design Code**

### **4.1 FSM**

```
module lab4_fsm (input logic clk, sa, sb, reset,
                output logic [2:0] la, logic [2:0] lb);

    // Slowed Clock
    //logic slower;
    //ClockDiv CD(clk(clk), .slow(slower));

    //Possible States
    typedef enum logic [2:0] {S0, S1, S2, S3, S4, S5, S6, S7} states; // all states are 3 bit
    states [2:0] current, next;

    // Lights
    parameter red_stop  = 3'b111;
    parameter green_go  = 3'b011;
    parameter yellow_wait = 3'b001;

    // Reset (CHANGE clk WITH slower TO SLOW THE CLOCK)!!!
    always_ff @(posedge clk, posedge reset)
    if (reset)
        current <= S0;
    else
        current <= next;

    // State Transition
    always_comb
    case (current)
        S0:
            if (sa)
                next = S0;
            else
                next = S1;
        S1:
            next = S2;
        S2:
            next = S3;
        S3:
            next = S4;
        S4:
```

```

        if (sb)
            next = S4;
        else
            next = S5;
    S5:
        next = S6;
    S6:
        next = S7;
    S7:
        next = S0;
endcase

```

// Output - State Matching

```

always_comb
case (current)
    S0:
        begin
            la = green_go;
            lb = red_stop;
        end
    S1:
        begin
            la = yellow_wait;
            lb = red_stop;
        end
    S2:
        begin
            la = red_stop;
            lb = red_stop;
        end
    S3:
        begin
            la = red_stop;
            lb = yellow_wait;
        end
    S4:
        begin
            la = red_stop;
            lb = green_go;
        end
    S5:
        begin
            la = red_stop;
            lb = yellow_wait;
        end
    S6:

```

```

        begin
            la = red_stop;
            lb = red_stop;
        end
    S7:
        begin
            la = yellow_wait;
            lb = red_stop;
        end
    endcase
endmodule

```

---

## **4.2 The Clock**

```

module ClockDiv( input logic clk, output logic slow );

```

```

    // Clock Counter
    logic [28:0] counter;

    always @( posedge clk )
    begin
        if( counter >= 199999999 )
        begin
            counter <= 0;
            slow  <= 0;
        end
        else
        begin
            counter <= counter + 1;
            slow  <= 1;
        end
    end
end

endmodule

```

---

## **5.0 SystemVerilog Testbench**

```

module testBench();

    // Parameters of the Finite State Machine
    logic clk, reset, sa, sb;
    logic [2:0] LA, LB;

    // Device Under Test
    lab4_fsm dut(clk(clk), .sa(sa), .sb(sb), .reset(reset), .la(LA), .lb(LB));

```



```

// Clock Signal
always
begin
    clk <= 1;      #5;
    clk <= 0;      #5;
end

initial
begin
    reset = 1;      #100; // beginnig

    reset = 0;

    sa = 0; sb = 0;  #100;
    sa = 0; sb = 1;  #100;
    sa = 1; sb = 0;  #100;
    sa = 1; sb = 1;  #100;

    reset = 1;

    sa = 0; sb = 0;  #40;
    sa = 0; sb = 1;  #40;
    sa = 1; sb = 0;  #40;
    sa = 1; sb = 1;  #40;
    $finish;
end

endmodule

```